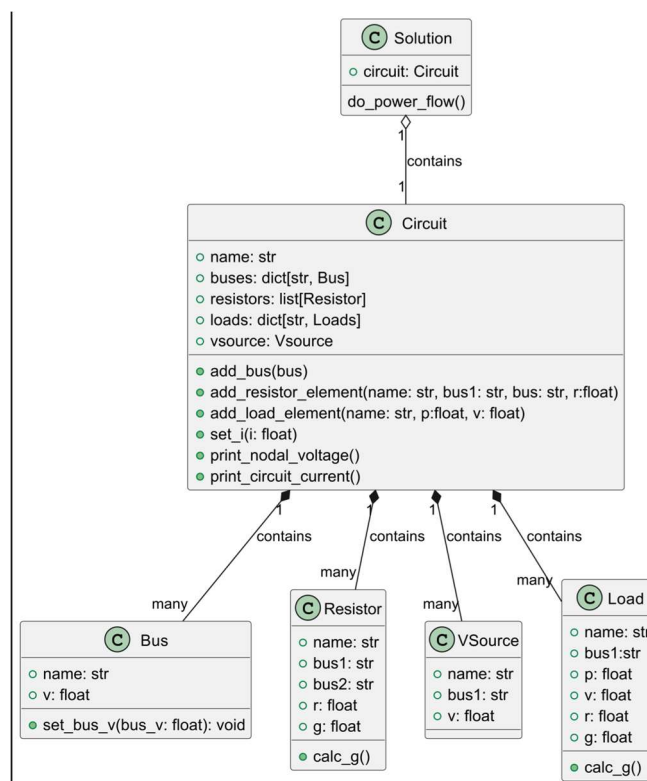


# ECE 1774 Project 1: Simple Circuit

## Overview:

The purpose of this project is to develop a Python script capable of simulating real-world power systems. I developed a Python model that solves a DC circuit consisting of a voltage source, series resistor, and load connected between two buses. While this model is currently limited to simulating this specific circuit, it serves as a foundational introduction to power system modeling capabilities and demonstrates the core object-oriented architecture that can be extended to more complex networks.

## Class Diagrams:



## Relevant Equations:

Ohms Law:  $V = IR$

Power-Voltage Relationship:  $P = IV = \frac{V^2}{R}$

Calculation conductance:  $G = \frac{1}{V} = \frac{1}{R}$

KVL Solution:

$$V_{source} - V_{resistor} - V_{load} = 0$$

$$V_a - I * R_{series} - V_b = 0$$

$$V_b = V_a - I * R_{series} = R_{load}$$

## Example Case:

To show the accuracy of the simulation, we will do an example test case using different values to validate the system under varying conditions. The circuit is composed of:

- Buses A and B
- Voltage source  $V_a$  connected at bus A with 200 V
- Resistor  $R_{ab}$  connected between buses A and B with 20 Ohms
- Load  $L_b$  connected to bus B with power of 300 W and nominal voltage of 100 V.

## Solution Process:

- 1) The voltage at the source directly sets the voltage at Bus A
- 2) For a constant impedance load model, the load resistance is calculated using the nominal voltage and power rating:

$$R_{load} = V_{nominal}^2 / P_{load} = (100)^2 / 3000 = 3.33 \Omega$$

- 3) The series resistor and load resistor form a series circuit:

$$R_{total} = R_{ab} + R_{load} = 20 + 3.33 = 23.33 \Omega$$

- 4) Using Ohm's Law with the total circuit resistance:

$$I = V_A / R_{total} = 200 / 23.33 = 8.57 \text{ A}$$

- 5) Using the voltage divider principle or Ohm's Law across the load:

$$V_B = I \times R_{load} = 8.57 \times 3.33 = 28.57 \text{ V}$$

### Simulation Results:

```
Nodal Voltages for Circuit: SimpleCircuit
```

```
Bus A: 200.00 V
```

```
Bus B: 28.57 V
```

```
Circuit Current for: SimpleCircuit
```

```
Current: 8.5714 A
```